

**DEPT. OF ELECTRICAL & ELECTRONICS ENGINEERING SRM
INSTITUTE OF SCIENCE AND TECHNOLOGY, Kattankulathur – 603203.**

Title of Experiment (a) PN junction diode, (b) Zener diode, (c)BJT	: 7. Characteristics of semiconductor devices
Name of the candidate	: Debarghya Barik
Register Number	: RA2011026010022
Date of Experiment	: 04.11.2020

Sl. No.	Marks Split up	Maximum marks (50)	Marks obtained
1	Pre Lab questions	5	
2	Preparation of observation	15	
3	Execution of experiment	15	
4	Calculation / Evaluation of Result	10	
5	Post Lab questions	5	
Total		50	

Staff Signature

PRE LAB QUESTIONS

1. What are intrinsic and extrinsic semiconductors?

Ans:

An **intrinsic semiconductor**, also called an undoped semiconductor or i-type semiconductor, is a pure semiconductor without any significant dopant species present.

An **extrinsic semiconductor** is one that has been doped that is impurities are intentionally added for making it conductive.

2. Give examples for Trivalent and Pentavalent impurity.

Ans:

Examples of **trivalent** impurities are boron, aluminium, and gallium.

Examples of **pentavalent** impurities are antimony, arsenic, phosphorus.

3. What is the need for Zener diode?

Ans:

Zener diodes are used for **voltage regulation**, as **reference elements**, **surge suppressors**, and in **switching applications** and **clipper circuits**. The load voltage equals breakdown voltage V_Z of the diode. The diode in series, resistor limits the current through the diode and drops the excess voltage when the diode is conducting. When connected in parallel with a variable voltage source so that it is reverse biased, a Zener diode conducts when the voltage reaches the diode's reverse breakdown voltage.

4. What is voltage regulation and mention its significance?

Ans:


Voltage regulation is a measure of change in the voltage magnitude between the sending and receiving end of a component, such as a transmission or distribution line. Voltage regulation describes the ability of a system to provide near constant voltage over a wide range of load conditions.

Significance: Change in load causes changes in current and hence the voltage drop in the circuit as well. It is necessary to maintain the supply voltage of the equipment because the supply voltage directly affects the performance of the equipment. Hence, the voltage regulation is significant.


5. Give the different types of semiconductor devices with symbols

Ans:


1. POWER DIODE:

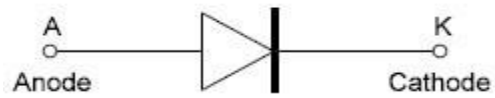


2.UNI JUNCTION TRANSISTOR:

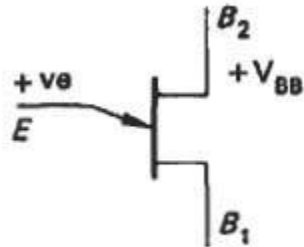


3.POWER BJT:

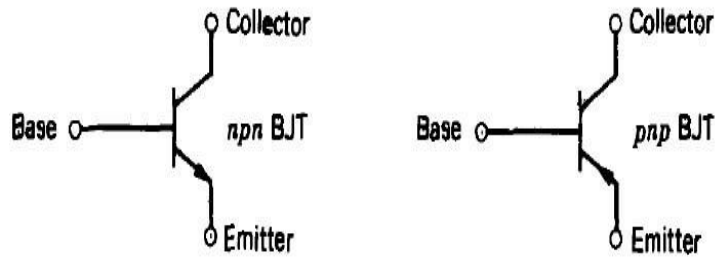

4.SILICON CONTROLLED RECTIFIER:

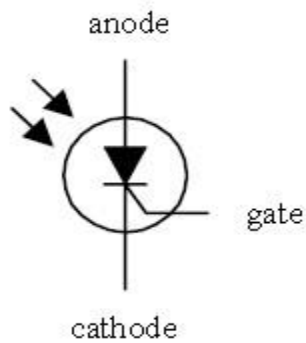

5.REVERSE CONDUCTING THYRISTOR:

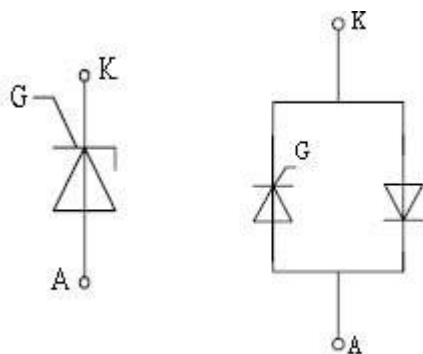**Experiment No. 7 a)****Date :** 04.11.2020**CHARACTERISTICS OF PN JUNCTION DIODE****Aim**

To study the characteristics of PN Junction diode under forward and reverse bias conditions.

Apparatus Required

S.No.	Name	Range	Qty
1	R.P.S	(0-30)V	1
2	Ammeter	(0-30)mA	1
		(0-500) μ A	1
3	Voltmeter	(0-1)V	1
		(0-10)V	1

Components Required

S.No.	Name	Range	Qty
1	Diode	IN4001	1
2	Resistor	1k Ω	1
3	Bread Board	-	1
4	connecting Wires	-	Req

Theory

A PN junction diode is a two terminal semiconducting device. It conducts only in one direction (only on forward biasing).

Forward Bias

On forward biasing, initially no current flows due to barrier potential. As the applied potential exceeds the barrier potential the charge carriers gain sufficient energy to cross the potential barrier and hence enter the other region. The holes, which are majority carriers in

the P-region, become minority carriers on entering the N-regions, and electrons which are the majority carriers in the N-region, become minority carriers on entering the P-region. This injection of minority carriers results in the current flow, opposite to the direction of electron movement.

Reverse Bias

On reverse biasing, the majority charge carriers are attracted towards the terminals due to the applied potential resulting in the widening of the depletion region. Since the charge carriers are pushed towards the terminals no current flows in the device due to majority charge carriers. There will be some current in the device due to the thermally generated minority carriers. The generation of such carriers is independent of the applied potential and hence the current is constant for all increasing reverse potential. This current is referred to as Reverse Saturation Current (I_0) and it increases with temperature. When the applied reverse voltage is increased beyond the certain limit, it results in breakdown.

During breakdown, the diode current increases tremendously.

Procedure Forward Bias

1. Connect the circuit as per the diagram.
2. Vary the applied voltage V in steps of 0.1V.
3. Note down the corresponding Ammeter readings I.
4. Plot a graph between V & I

Observations

1. Find the d.c (static) resistance = V/I .
2. Find the a.c (dynamic) resistance $r = \Delta V / \Delta I$ ($r = \Delta V / \Delta I = (V_2 - V_1) / (I_2 - I_1)$)
3. Find the forward voltage drop [Hint: it is equal to 0.7 for Si and 0.3 for Ge]

Reverse Bias

1. Connect the circuit as per the diagram.
2. Vary the applied voltage V in steps of 1.0V.
3. Note down the corresponding Ammeter readings I.
4. Plot a graph between V & I


5. Find the dynamic resistance $r = \Delta V / \Delta I$.

Formula for Reverse Saturation Current (I_0):


$$I = I_0(e^{(V/\eta V_T)} - 1)$$

where I is forward (or reverse) diode current, I_0 is reverse saturation current, V is external voltage (+ve for forward bias & -ve for reverse bias), η is constant number (1 for Silicon and 2 for Germanium), V_T is the volt-equivalent of temperature ($T/11600$) and T is temperature in Kelvin. **Circuit Diagram**

Forward Bias

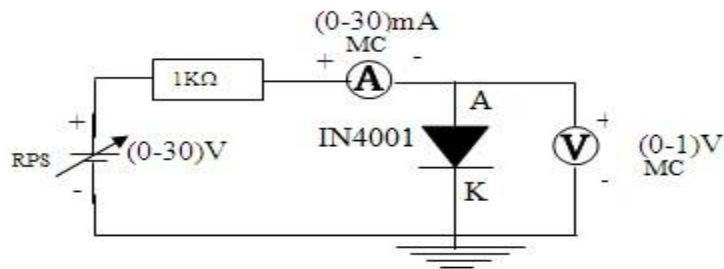

Reverse Bias

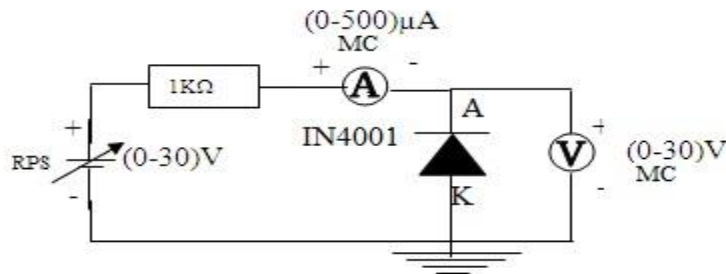

Specification for 1N4001: Silicon Diode


Peak Inverse Voltage: 50V

$I_{dc} = 1A$.


Maximum forward voltage drop at 1 Amp is 1.1 volts

Maximum reverse current at 50 volts is $5\mu A$

Forward Bias:

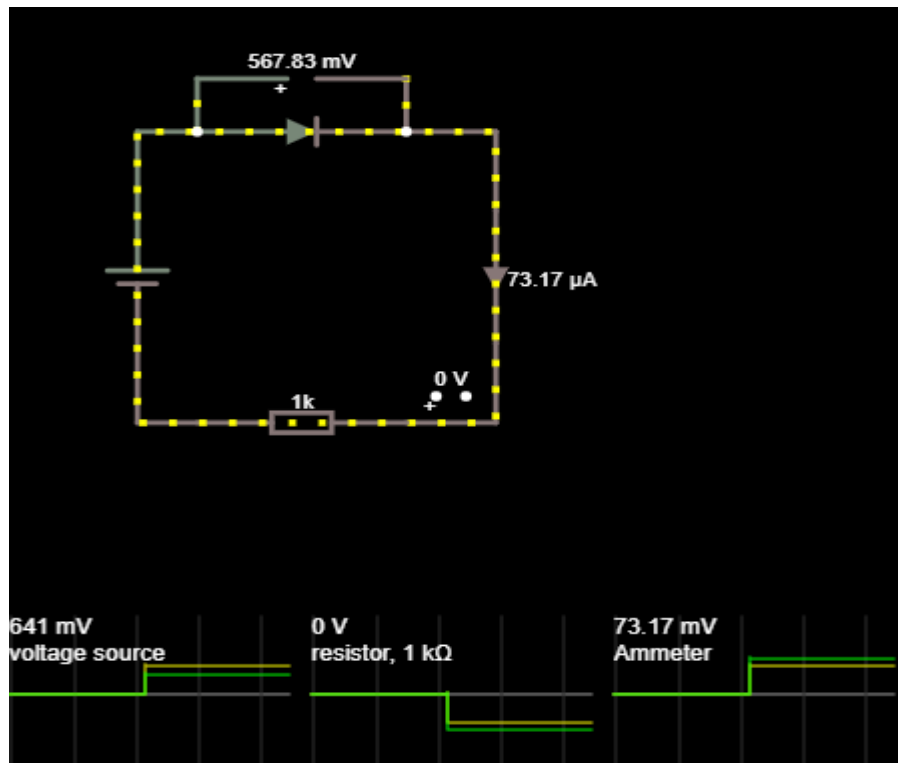

Reverse Bias:

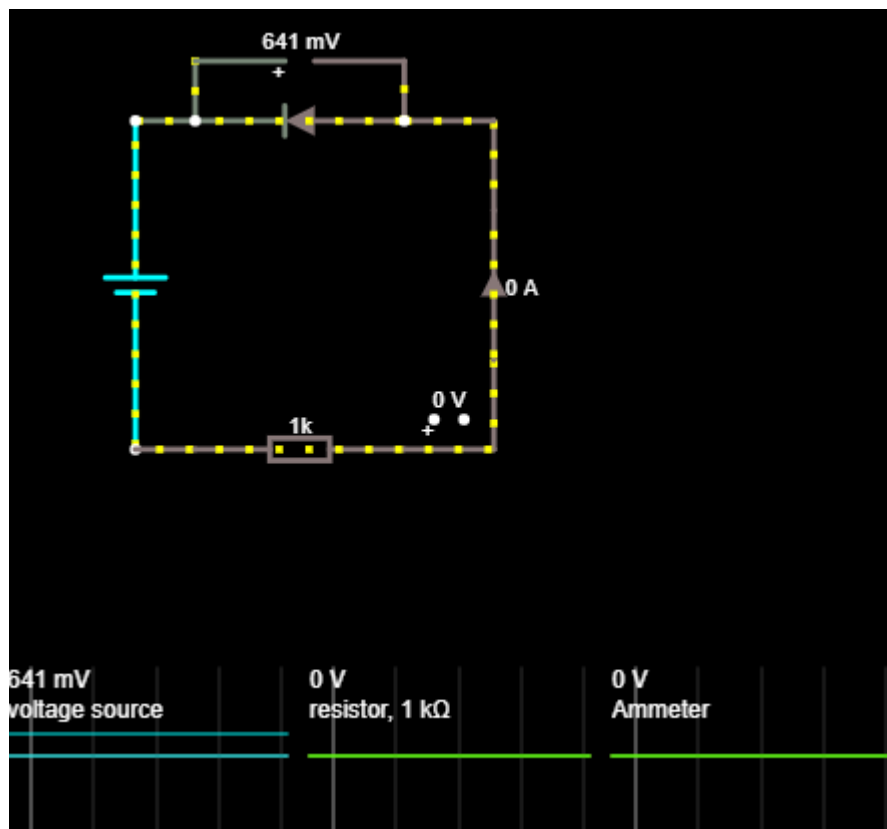


Tabular Column**Forward Bias**


S.No.	Voltage V_f (In Volts)	Current I_f (In mA)
1.	0.641	1.36
2.	0.670	4.33
3.	0.689	9.31
4.	0.700	14.30
5.	0.705	19.29
6.	0.713	24.29
7.	0.718	29.28

Reverse Bias

S.No.	Voltage V_r (In Volts)	Current I_r (In μA)
1.	2	0
2.	5	0
3.	10	0
4.	15	0
5.	20	0
6.	25	0
7.	30	0

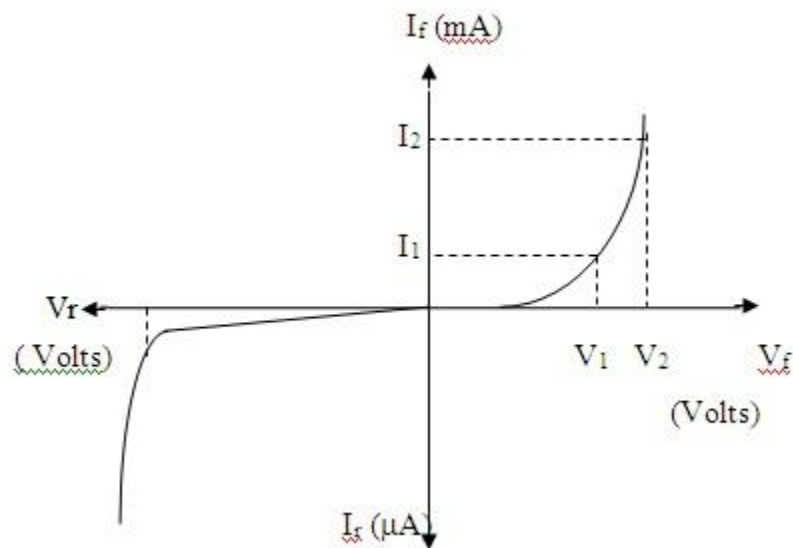Model Graph

Diode Graph:

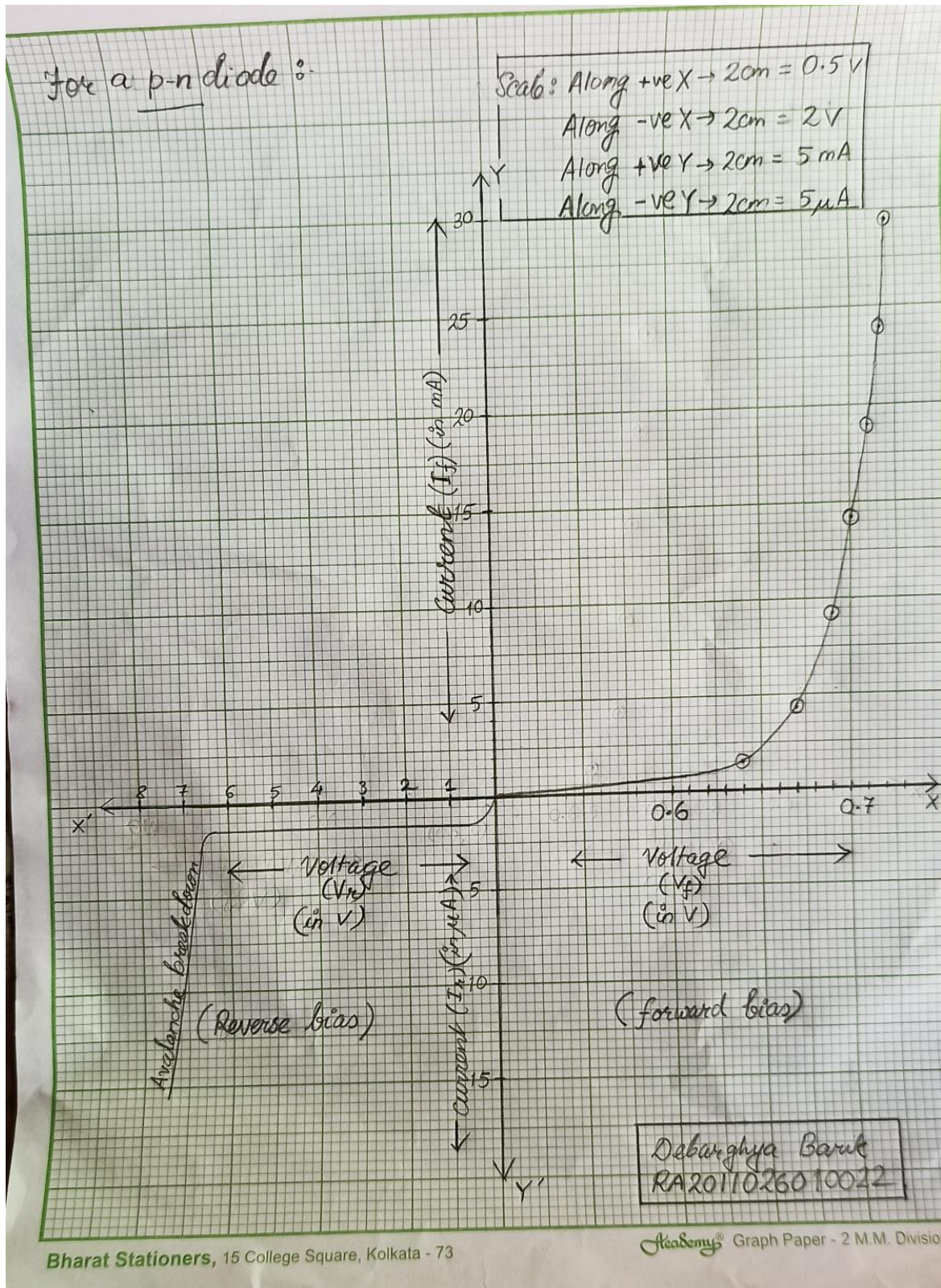

Result : From the experiment it is concluded that under reverse biasing of diode the resistance is infinite and thus no current flows through it but when large voltage is applied the current overcomes the potential barrier and the value becomes infinite. In case of a forward biased diode it is noticed that current passes through it and there is an exponential increase in current as voltage is increased.

Experiment No. 7 b) Date : 04.11.2020	CHARACTERISTICS OF ZENER DIODE
--	---------------------------------------

Aim

To find the forward and reverse bias characteristics of a given Zener diode.

Apparatus Required

S.No.	Name	Range	Qty
1	R.P.S	(0-30)V	1s
2	Ammeter	(0-30)mA	2
3	Voltmeter	(0-10)V	1
		(0-1)V	1

Components Required

S.No.	Name	Range	Qty
1	Zener diode	FZ5.1	1
2	Resistor	1K Ω	1
3	Bread Board	-	1
4	Wires	-	Req

Theory

A properly doped crystal diode, which has a sharp breakdown voltage, is known as Zener diode.

Forward Bias

On forward biasing, initially no current flows due to barrier potential. As the applied potential increases, it exceeds the barrier potential at one value and the charge carriers gain sufficient energy to cross the potential barrier and enter the other region. The holes, which are majority carriers in p-region, become minority carriers on entering the N regions and electrons, which are the majority carriers in the N-regions become minority carriers on entering the P-region. This injection of minority carriers results current, opposite to the direction of electron movement.

Reverse Bias

When the reverse bias is applied, due to majority carriers small amount of current (i.e.,) reverse saturation current flows across the junction. As the reverse bias is increased to breakdown voltage, sudden rise in current takes place due to Zener effect.

Zener Effect

Normally, PN junction of Zener Diode is heavily doped. Due to heavy doping the depletion layer will be narrow. When the reverse bias is increased the potential across the depletion layer is more. This exerts a force on the electrons in the outermost shell. Because of this force the electrons are pulled away from the parent nuclei and become free electrons. This ionization, which occurs due to electrostatic force of attraction, is known as **Zener effect**. It results in large number of free carriers, which in turn increases the reverse saturation current.

Procedure Forward Bias


1. Connect the circuit as per the circuit diagram.
2. Vary the power supply in such a way that the readings are taken in steps of 0.1V in the voltmeter till the needle of power supply shows 30V.
3. Note down the corresponding ammeter readings.
4. Plot the graph between V & I.
5. Find the dynamic resistance $r = \Delta V / \Delta I$.

Reverse Bias


1. Connect the circuit as per the diagram.
2. Vary the power supply in such a way that the readings are taken in steps of 0.1V in the voltmeter till the needle of power supply shows 30V.
3. Note down the corresponding Ammeter readings I.
4. Plot a graph between V & I
5. Find the dynamic resistance $r = \delta V / \delta I$.
6. Find the reverse voltage V_r at $I_z = 20\text{mA}$

Circuit Diagram


Forward Bias

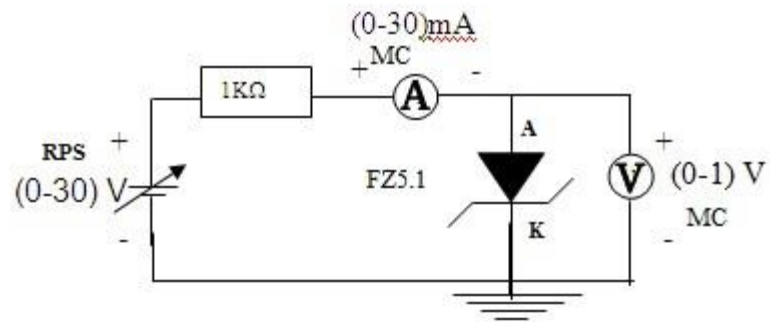


Reverse Bias

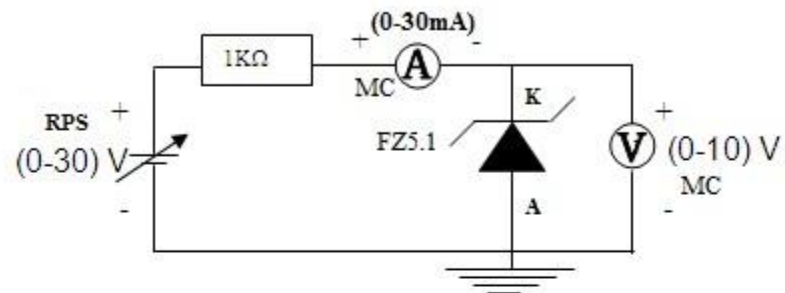


Zener Diode

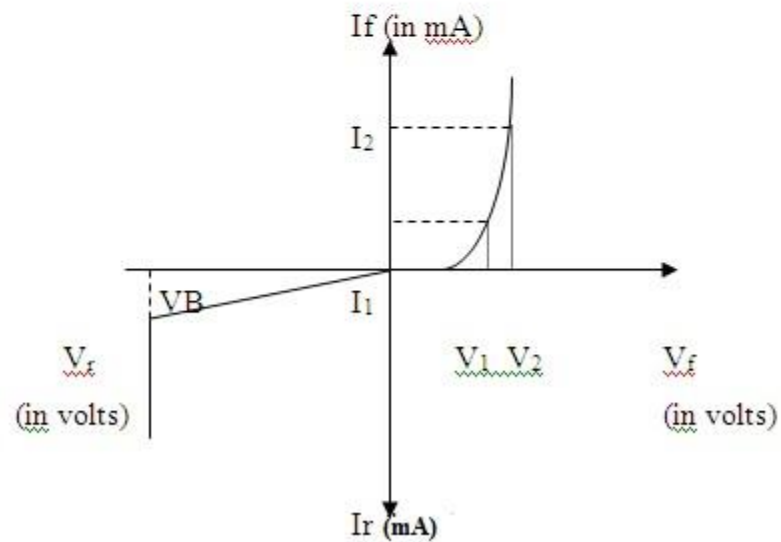

Forward Bias:

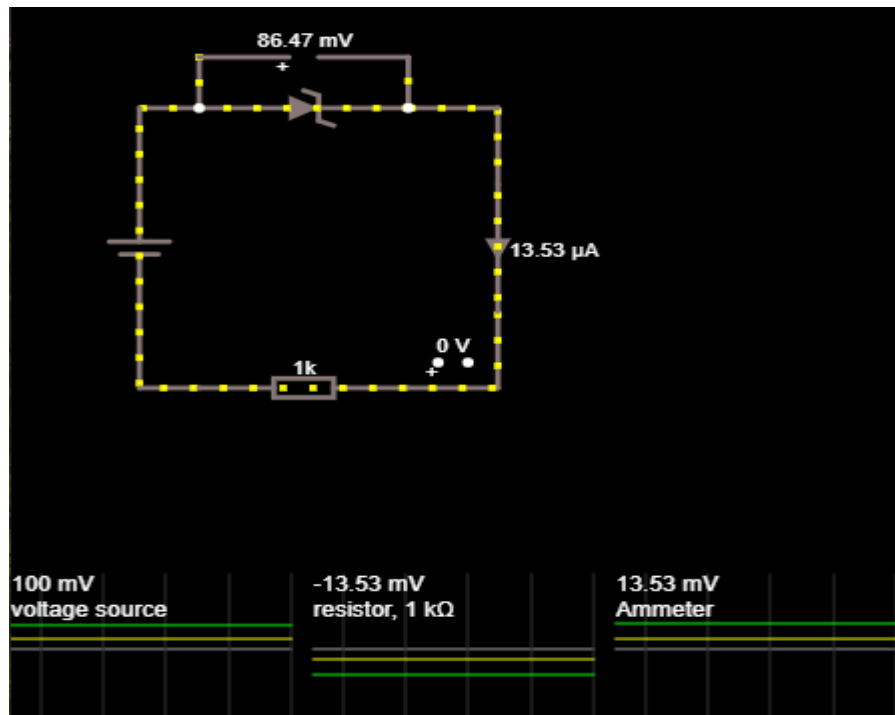

Reverse Bias:

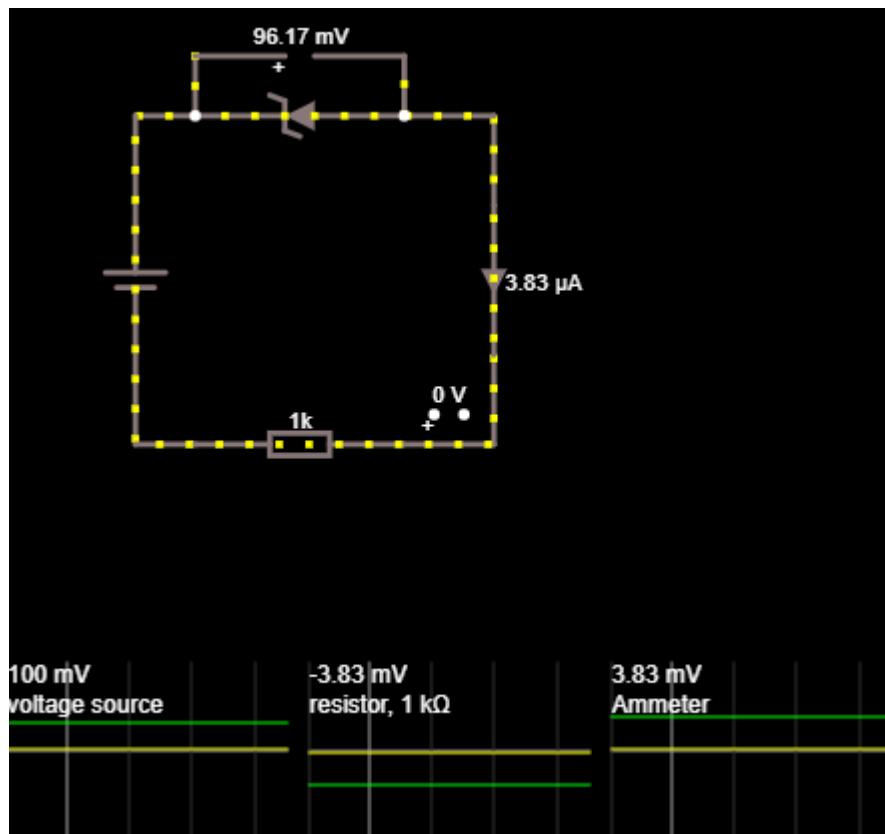

Tabular Column

Forward Bias			Reverse Bias		
S.No.	Voltage (In Volts)	Current (In uA)	S.No.	Voltage (In Volts)	Current (In uA)
1	0.1	13.5	1	0.1	3.8
2	0.2	46.3	2	0.2	4.7
3	0.3	99.4	3	0.3	4.9
4	0.4	166.6	4	0.4	5
5	0.5	242.4	5	0.5	5
6	0.6	323.6	6	0.6	5
7	0.7	408.5	7	0.7	5
8	0.8	495.8	8	0.8	5
9	0.9	585.0	9	0.9	5
10	1.0	675.6	10	1.0	5

THEORETICAL VALUES**FORWARD BIAS(ZENER)**

- Dynamic resistance= $\Delta V / \Delta I = 1.01 \text{ ohm}$

REVERSE BIAS (ZENER)

- AC resistance= $\Delta V / \Delta I = 1.02 \text{ ohm}$
- Voltage V_r at $I_z = 20 \text{ mA}$ for 0.0013 V


$$I_o = I_s [e^{aV_d / NkT} - 1]$$

$$S/R = 20 [e^{-1.6 \times 10^{-14} \cdot V_d / 2 \cdot 295 \cdot K} - 1]$$

$$1.025 = e^{-19.65 V_d}$$

$$V_d = -1.257 \times 10^{-3} \text{ V}$$

Zener Diode Graph:

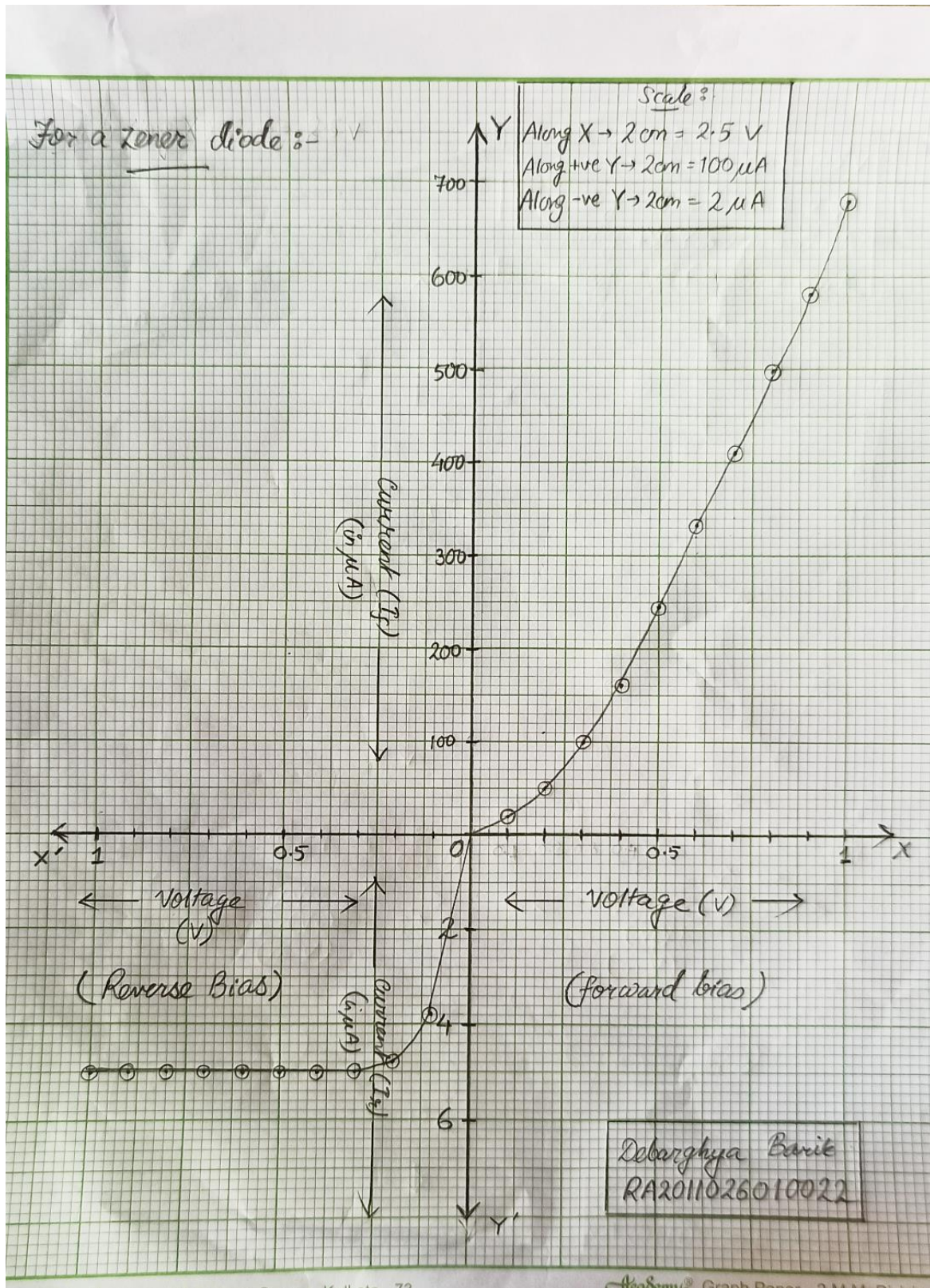

Result : In case of forward biased Zener diode it is observed that there is gradual increase in current as voltage is increased. In case of reverse biased Zener diode at starting there is increment in value of current but after some time the value of current remains unchanged for a long period of values then when the value of voltage is further increased then it is observed that there is an exponential rise in current too.

-----X-----