

DEPT. OF ELECTRICAL & ELECTRONICS ENGINEERING  
SRM INSTITUTE OF SCIENCE AND TECHNOLOGY, Kattankulathur – 603 203

Title of Experiment	: <b>1. Verification of Kirchhoff's Laws</b>
Name of the candidate	:
Register Number	:
Date of Experiment	:

Sl. No.	Marks Split up	Maximum marks (50)	Marks obtained
1	Pre Lab questions	5	
2	Preparation of observation	15	
3	Execution of experiment	15	
4	Calculation / Evaluation of Result	10	
5	Post Lab questions	5	
<b>Total</b>		<b>50</b>	

Staff Signature

## PRE LAB QUESTIONS

- 1. Define Ohm's law.**
- 2. State KCL and KVL.**
- 3. Define absolute potential and potential difference**
- 4. What is the difference between mesh and loop?**
- 5. What is super-node?**

Experiment No. 1 Date :	VERIFICATION OF KIRCHHOFF'S LAWS
----------------------------	----------------------------------

**Aim:**

To verify Kirchhoff's current law and Kirchhoff's voltage law for the given circuit.

**Apparatus Required:**

Sl.No	Apparatus	Range	Quantity
1	RPS (regulated power supply)	(0-30V)	2
2	Resistance	330Ω, 220Ω 1kΩ	6
3	Ammeter	(0-30mA)MC	3
4	Voltmeter	(0-30V)MC	3
5	Bread Board & Wires	--	Required

**Statement:**

**KCL:** The algebraic sum of the currents meeting at a node/junction is equal to zero.

**KVL:** In any closed path / mesh, the algebraic sum of all the voltages is zero.

**Precautions:**



1. Voltage control knob should be kept at minimum position.
2. Current control knob of RPS should be kept at maximum position.

**Procedure for KCL:**

1. Give the connections as per the circuit diagram.
2. Set a particular value in RPS.
3. Note down the corresponding ammeter reading
4. Repeat the same for different voltages

**Procedure for KVL:**

1. Give the connections as per the circuit diagram.
2. Set a particular value in RPS.
3. Note all the voltage reading
4. Repeat the same for different voltages

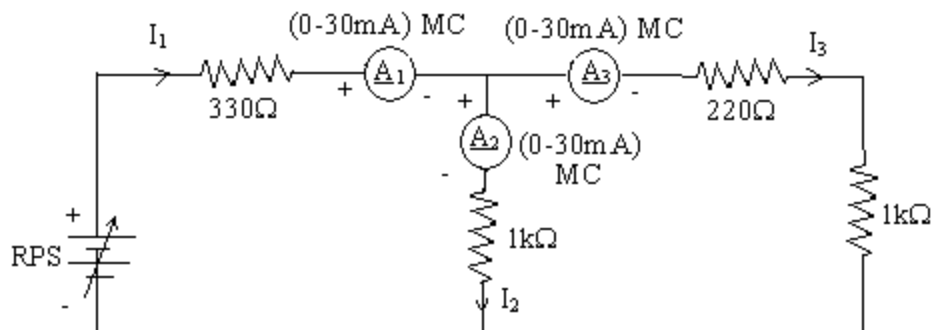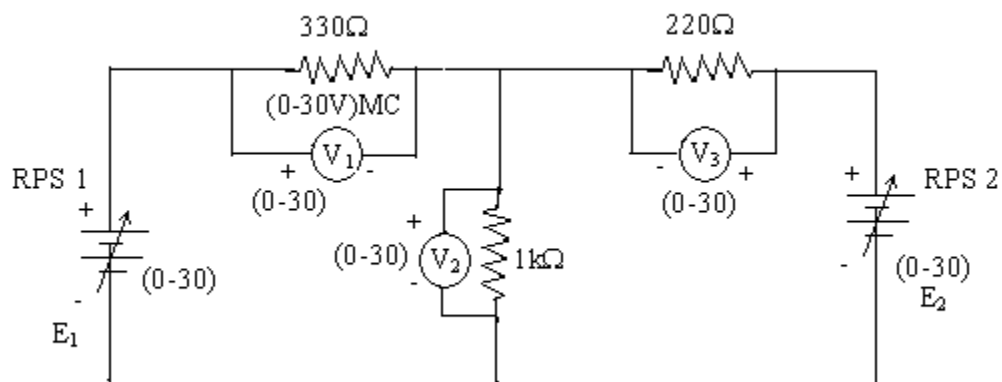**HARDWARE SETUP:****Circuit for KCL verification:****Circuit for KVL verification:****KCL - Theoretical Values:**

Sl. No.	Voltage E Volts	Current			$I_1 = I_2 + I_3$ mA
		$I_1$ mA	$I_2$ Ma	$I_3$ mA	
1	5	0.00568	0.00312	0.00256	0.00568
2					
3					
4					
5					

**KCL - Practical Values:**

Sl. No.	Voltage E Volts	Current			$I_1 = I_2 + I_3$ mA
		$I_1$ mA	$I_2$ mA	$I_3$ mA	
1	5	33.33	16.66	16.67	33.33
2					
3					

**KVL – Theoretical Values**

Sl.No	RPS		Voltage			KVL $E_1 = V_1 + V_2$
	$E_1$	$E_2$	$V_1$	$V_2$	$V_3$	
	V	V	V	V	V	V
1						
2						
3						
4						
5						

**KVL - Practical Values**

Sl.No	RPS		Voltage			KVL $E_1 = V_1 + V_2$
	$E_1$	$E_2$	$V_1$	$V_2$	$V_3$	
	V	V	V	V	V	V
1						
2						
3						

**Model Calculations:**

**Result:**

**POST LAB QUESTIONS**

- 1) Illustrate KCL and KVL.**
- 2) Express the limitations of Ohm's law?**
- 3) What is the practical application of Kirchhoff's law?**
- 4) Compare series and parallel circuits**
- 5) What is the difference between series and parallel connection of batteries?**