

DEPT. OF ELECTRICAL & ELECTRONICS ENGINEERING

SRM INSTITUTE OF SCIENCE AND TECHNOLOGY, Kattankulathur – 603 203

Title of Experiment	: 2. VERIFICATION OF ALL THEOREMS- (THEVENIN, NORTON, MAXIMUM POWER TRANSFER)
Name of the candidate	:
Register Number	:
Date of Experiment	:

Sl. No.	Marks Split up	Maximum marks (50)	Marks obtained
1	Pre Lab questions	5	
2	Preparation of observation	15	
3	Execution of experiment	15	
4	Calculation / Evaluation of Result	10	
5	Post Lab questions	5	
Total		50	

Staff Signature

PRE LAB QUESTIONS

- 1. Define Lumped and distributed elements.**
- 2. State Thevenin's theorem?**
- 3. State Norton's theorem?**
- 4. List the applications of Thevenin's and Norton's theorems?**
- 5. What are the different types of dependent or controlled sources?**

Experiment No. 2 a) Date :	THEVENIN'S THEOREM
-------------------------------	--------------------

Aim:

To verify Thevenin's theorem and to find the full load current for the given circuit.

Apparatus Required:

Sl.No.	Apparatus	Range	Quantity
1	RPS (regulated power supply)	(0-30V)	2
2	Ammeter	(0-10mA)	1
3	Resistors	1K Ω , 330 Ω	3,1
4	Bread Board	--	Required
5	DRB	--	1

Statement:

Any linear bilateral, active two terminal network can be replaced by a equivalent voltage source (V_{TH}). Thevenin's voltage or V_{OC} in series with looking back resistance R_{TH} .

Precautions:

1. Voltage control knob of RPS should be kept at minimum position.
2. Current control knob of RPS should be kept at maximum position

Procedure:

1. Connections are given as per the circuit diagram.
2. Set a particular value of voltage using RPS and note down the corresponding ammeter readings.

To find V_{TH}

3. Remove the load resistance and measure the open circuit voltage using multimeter (V_{TH}).


To find R_{TH}

4. To find the Thevenin's resistance, remove the RPS and short circuit it and find the R_{TH} using multimeter.
5. Give the connections for equivalent circuit and set V_{TH} and R_{TH} and note the corresponding ammeter reading.
6. Verify Thevenins theorem.


Theoretical and Practical Values

	E(V)	$V_{TH}(V)$	$R_{TH}(\Omega)$	$I_L (mA)$	
				Circuit - I	Equivalent Circuit
Theoretical					
Practical					


Circuit - 1 : To find load current

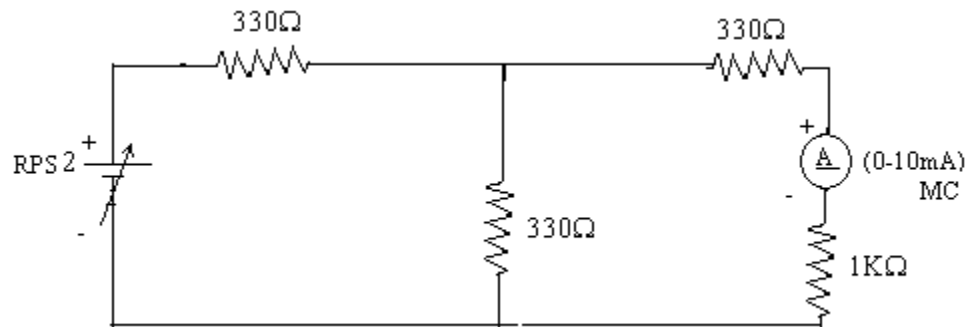


To find V_{TH}

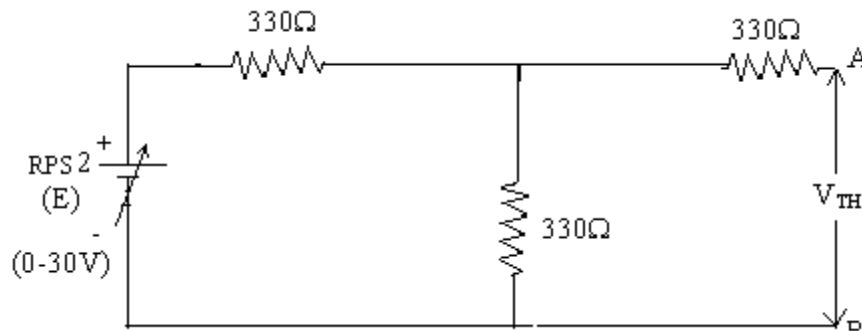

To find R_{TH}

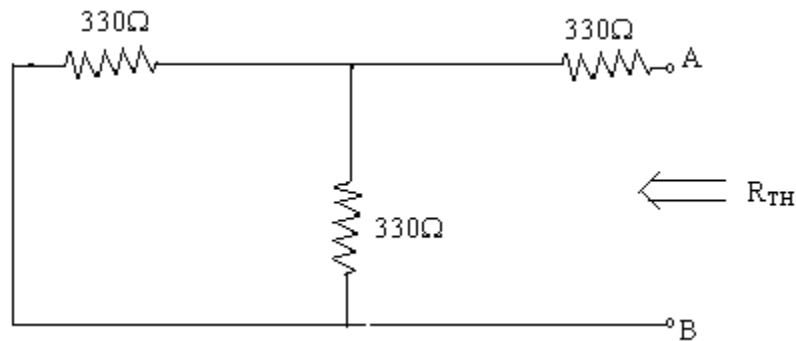

Thevenin's Equivalent circuit:

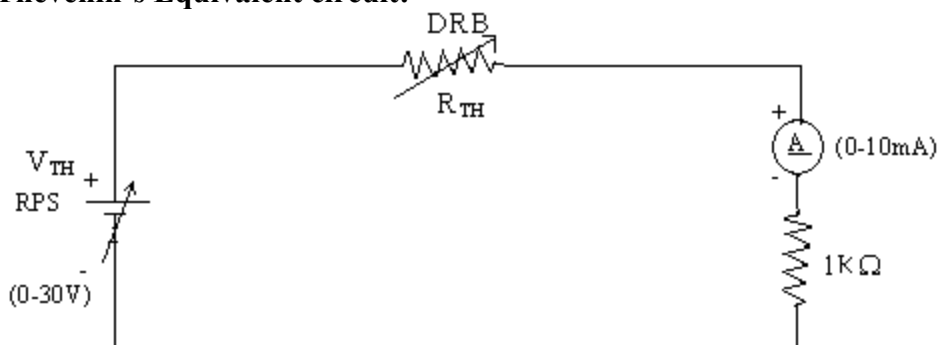

Model Calculations:

Result:

Experiment No. 2 b) Date :	VERIFICATION OF NORTON'S THEOREM
---	---

Aim:

To verify Norton's theorem for the given circuit.

Apparatus Required:

Sl.No.	Apparatus	Range	Quantity
1	Ammeter	(0-10mA) MC (0-30mA) MC	1 1
2	Resistors	330, 1K Ω	3,1
3	RPS	(0-30V)	2
4	Bread Board	--	1
5	Wires	--	Required

Statement:

Any linear, bilateral, active two terminal network can be replaced by an equivalent current source (I_N) in parallel with Norton's resistance (R_N)

Precautions:

1. Voltage control knob of RPS should be kept at minimum position.
2. Current control knob of RPS should be kept at maximum position.

Procedure:

1. Connections are given as per circuit diagram.
2. Set a particular value in RPS and note down the ammeter readings in the original circuit.

To Find I_N :

3. Remove the load resistance and short circuit the terminals.
4. For the same RPS voltage note down the ammeter readings.


To Find R_N :

5. Remove RPS and short circuit the terminal and remove the load and note down the resistance across the two terminals.


Equivalent Circuit:

6. Set I_N and R_N and note down the ammeter readings.
7. Verify Norton's theorem.


To find load current in circuit 1:

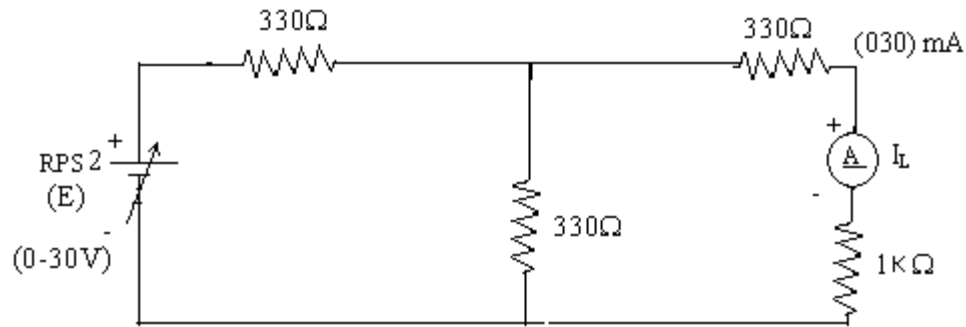


To find I_N

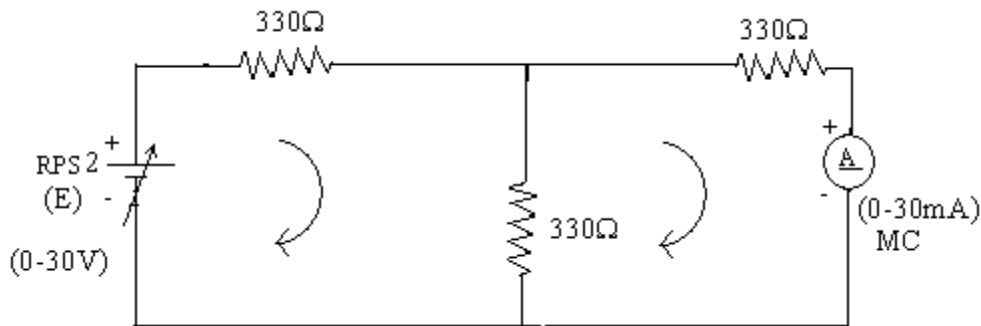

To find R_N

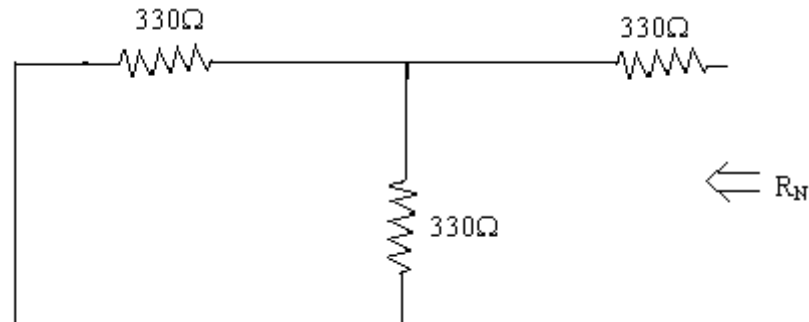

Norton's equivalent circuit

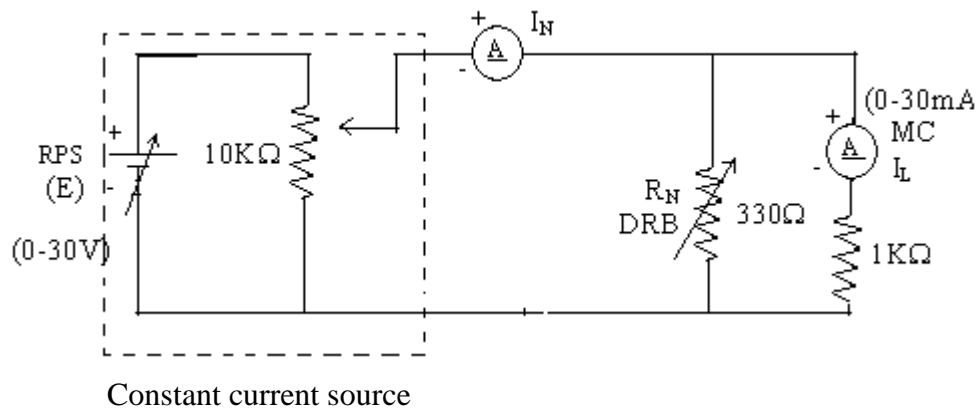

Theoretical and Practical Values

	E (volts)	I_N (mA)	R_N (Ω)	I_L (mA)	
				Circuit - I	Equivalent Circuit
Theoretical Values					
Practical Values					

Model Calculations:**Result:**

Experiment No. 2 c) Date :	VERIFICATION OF MAXIMUM POWER TRANSFER THEOREM
-------------------------------	--

Aim:

To verify maximum power transfer theorem for the given circuit

Apparatus Required:

Sl.No.	Apparatus	Range	Quantity
1	RPS	(0-30V)	1
2	Voltmeter	(0-10V) MC	1
3	Resistor	1K Ω , 1.3K Ω , 3 Ω	3
4	DRB	--	1
5	Bread Board & wires	--	Required

Statement:

In a linear, bilateral circuit the maximum power will be transferred from source to the load when load resistance is equal to source resistance.

Precautions:

1. Voltage control knob of RPS should be kept at minimum position.
2. Current control knob of RPS should be kept at maximum position.

Procedure:**Circuit – I**

1. Connections are given as per the diagram and set a particular voltage in RPS.
2. Vary R_L and note down the corresponding ammeter and voltmeter reading.
3. Repeat the procedure for different values of R_L & Tabulate it.
4. Calculate the power for each value of R_L .

To find V_{TH} :

5. Remove the load, and determine the open circuit voltage using multimeter (V_{TH})


To find R_{TH} :

6. Remove the load and short circuit the voltage source (RPS).
7. Find the looking back resistance (R_{TH}) using multimeter.


Equivalent Circuit:

8. Set V_{TH} using RPS and R_{TH} using DRB and note down the ammeter reading.
9. Calculate the power delivered to the load ($R_L = R_{TH}$)
10. Verify maximum transfer theorem.


Circuit - 1

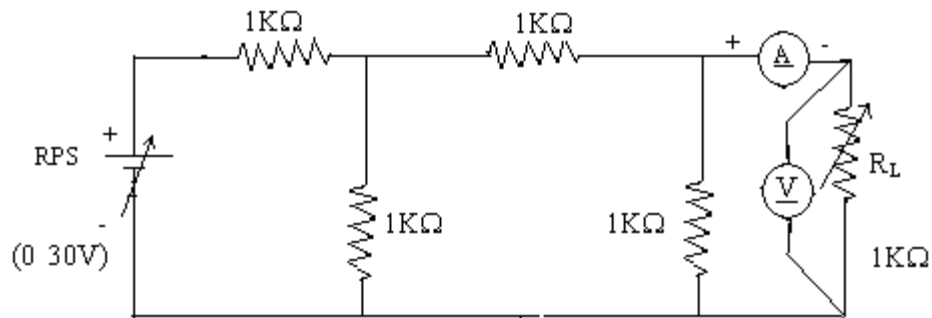


To find V_{TH}

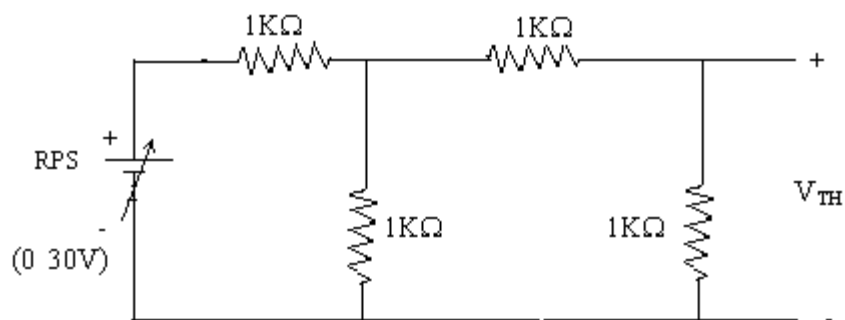


To find R_{TH}

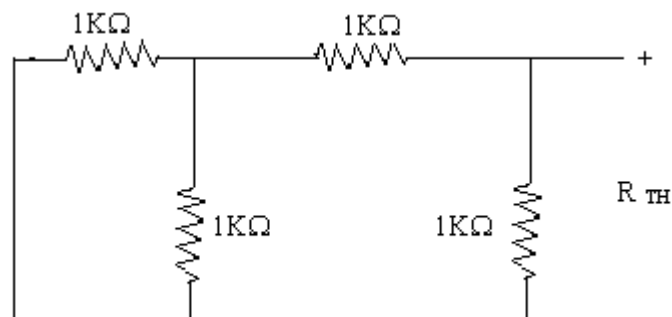

Thevenin's Equation Circuit

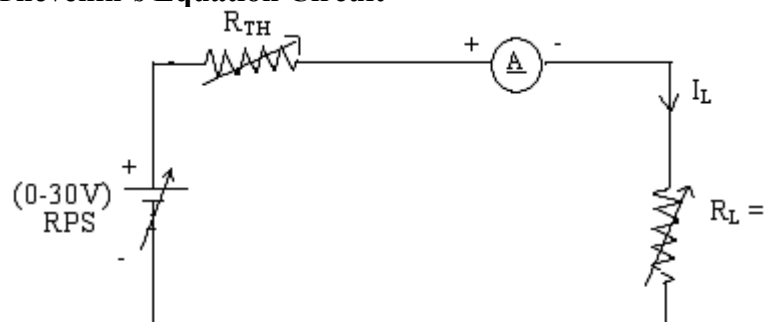

Power $V_S R_L$

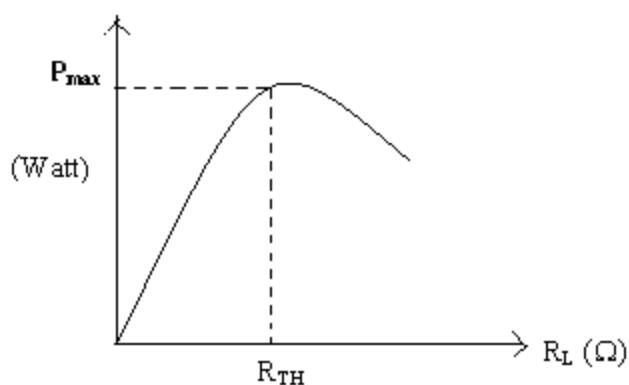

Circuit – I


Sl.No.	$R_L (\Omega)$	I (mA)	V(V)	$P=VI$ (watts)

To find Thevenin's equivalent circuit

	V_{TH} (V)	R_{TH} (Ω)	I_L (mA)	P (milli watts)
Theoretical Value				
Practical Value				

Model Calculations:

GRAPH:

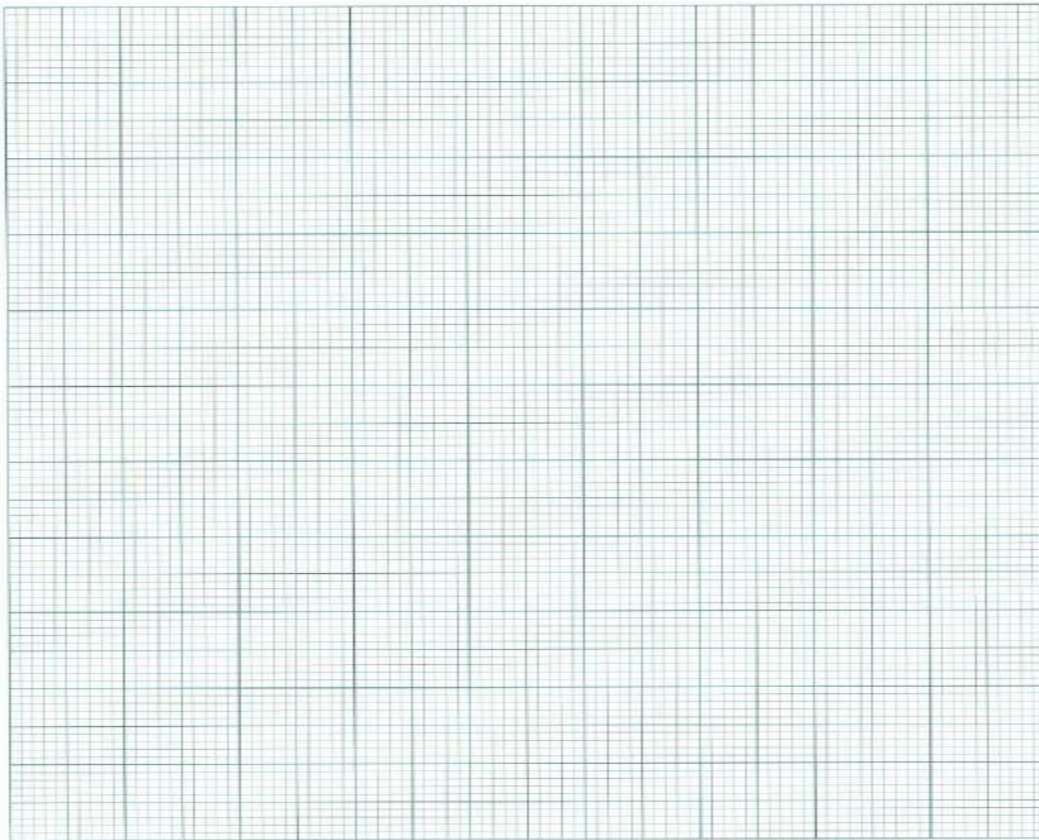

Result:

POST LAB QUESTIONS

- 1. State Thevenin's Theorem.**
- 2. Draw the Thevenin's equivalent circuit**
- 3. State maximum power transfer theorem.**
- 4. Write some applications of maximum transfer theorem.**
- 5. Write the steps to find I_N**
- 6. What are the steps to solve Maximum power transfer Theorem?**