

University Practical  
(BEEE)

Debaghya Barik.  
RA2011026010022


Q22 >

AIM: To study the clipping circuits for different reference voltages and to verify the responses in order to clip the negative cycle of 1 kHz input under unbiased condition and obtain the output voltage across the load.

APPARATUS:


SL.No	Name	Range	Qty
1	CRO	1 Hz - 20 MHz	1
2.	RPS	(0-30)V	1
3.	Bread Board	-	1
4.	Connecting wires	-	Req.
5.	Function Generator	1 Hz - 1 MHz	1
6.	Resistor	10 k Hz	1
7.	Diode	1N4007	1

## Circuit Diagram:-

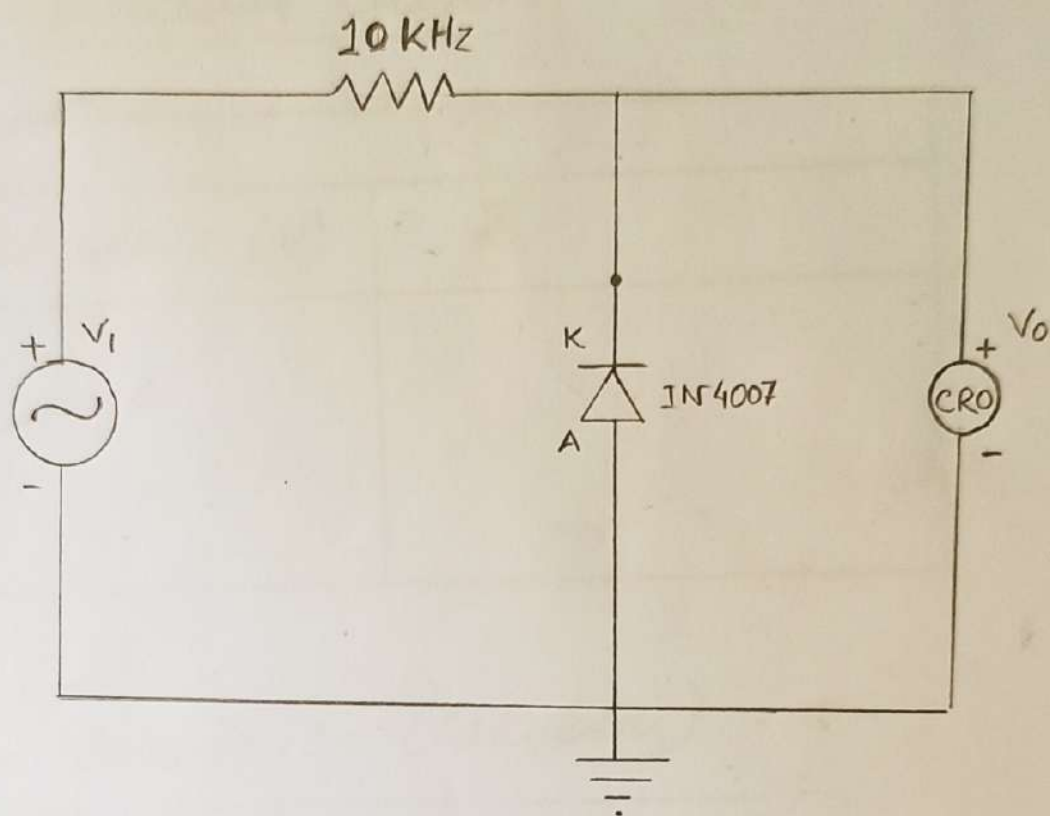


## Model Graph :-

### Input Waveform

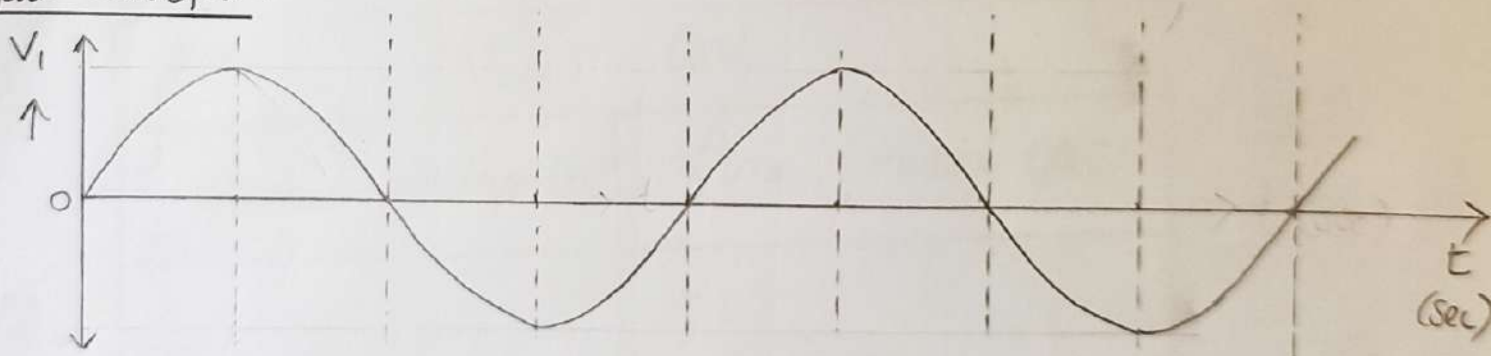

### Unbiased Clipper Output waveform.

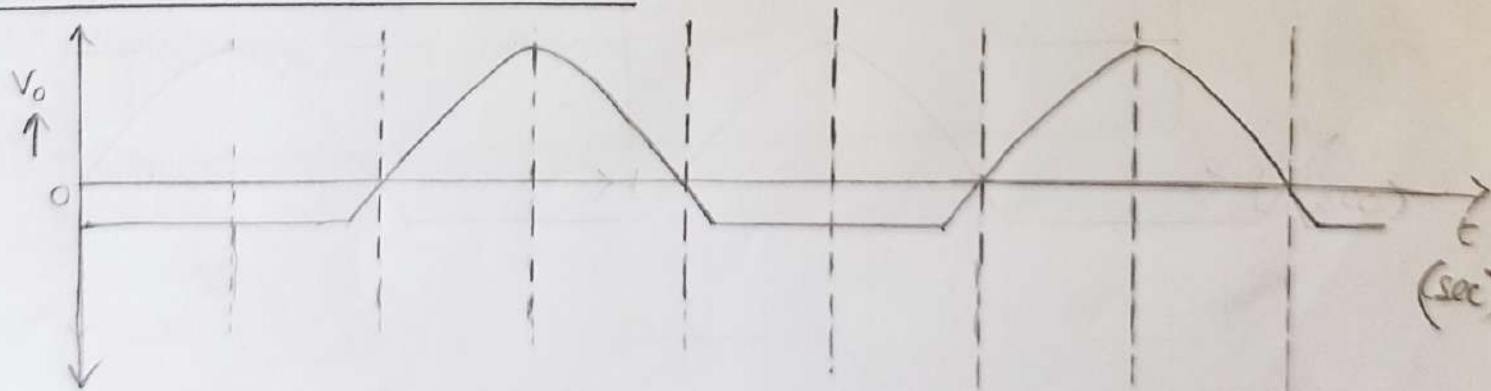

Tabular Column :- (calculation)

Unbiased Negative Clipper :

$V_{ref} = 0V$	
Output Voltage (mV)	Time Period ( $\mu s$ )
-612.61	5



Result : The characteristics of unbiased clipper are studied from the e-circuit simulation and the graph. Here the negative cycle of 1 KHz input voltage is clipped using an unbiased clipper.


ViVa :

Ans 1 > Clippers can be used as:-


- For generation of new waveforms or shaping the existing waveform.
- It is used as a protection of transistor from transients
- The excessive noise spikes above the certain level can be limited or clipped in FM transmitters by using series clippers.
- They are frequently used for the separation of synchronizing signals from composite picture signals.

Ans 2 > The frequency of a sine wave is the number of complete cycles that happen every second i.e. in other words, it is the number of waves that ~~passed~~ pass a fixed point in unit time.

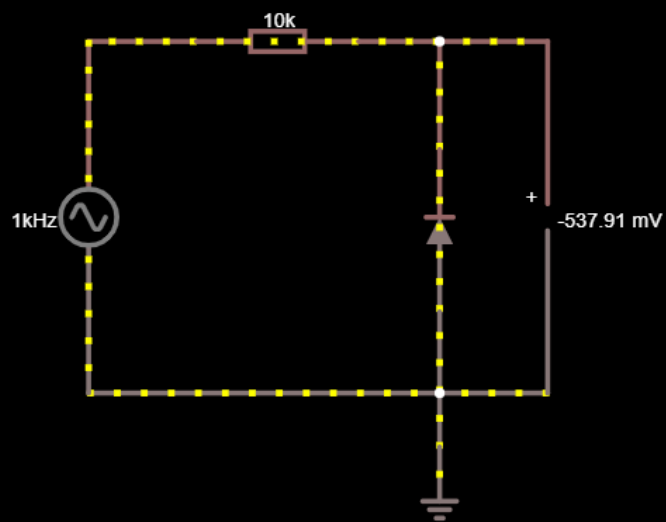The time period of a sinusoidal wave is the time taken to complete one revolution ( $T$ ). In other words, it is the length of one cycle of the curve. It is related to the frequency as  $T = \frac{1}{f}$ .



5 V  
voltmeter

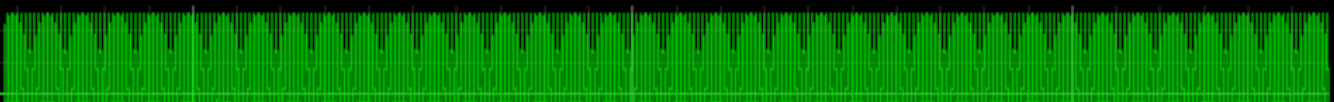

t = 3.96 s  
time step = 5  $\mu$ s



Ans 2) The figure

